

**Bachelor of Science (B.Sc. I.T.) Semester—II Examination****FUNDAMENTALS OF DIGITAL ELECTRONICS****Paper—I**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :—** (1) **ALL** questions are compulsory.

(2) Draw a well labelled diagram wherever necessary.

**EITHER**

1. (A) Explain the method to convert the real decimal number into binary with suitable example. 5
- (B) Explain the various methods to represent the negative binary numbers. 5

**OR**

- (C) Explain the weighted and unweighted binary codes. State the advantages of weighted codes. 5
- (D) Do as directed :

(i)  $(11001)_{\text{binary}} = ( )_{\text{Grey}}$

(ii)  $(1001)_{\text{binary}} = ( )_{\times 3}$

(iii)  $(175.2)_8 = ( )_{10}$

(iv)  $(121)_{10} = ( )_{16}$

(v)  $(134)_{10} = ( )_{\text{BCD}}$  5

**EITHER**

2. (A) Explain XOR and XNOR gates using logic circuit and truth table. 5
- (B) What is K-Map ? State rules for simplification and expression using K-Map. 5

**OR**

- (C) Solve by using K-Map :

$$f(A, B, C, D) = \Sigma m(0, 1, 2, 3, 8, 9, 10, 11).$$
 5


- (D) State and prove DeMorgan's theorem using logic gates. 5

**EITHER**

3. (A) Explain the working of 4 : 1 MUX. Design 4 : 1 MUX using 2 : 1 MUX. 5
- (B) Explain the working of binary counter with suitable diagram. 5

**OR**

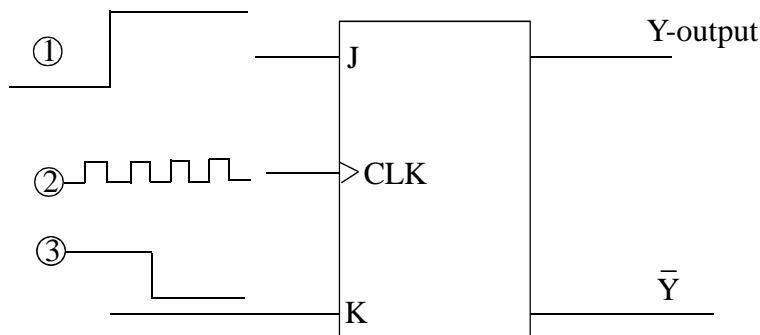- (C) What is race around condition ? How it is eliminated ? Explain. 5
- (D) Explain RS Flip-Flop using NOR gate. Draw the waveform at Y output. 5



**EITHER**

4. (A) Classify the memory on the basis of speed and storage. Explain. 5
- (B) Explain the construction and working of Hard Disk. 5

**OR**

- (C) Explain any two I/O devices. 5
- (D) Explain the fastest memory used in the computer. 5
5. (A) Explain alphanumeric code. 2½
- (B) Standardise the given expression for K-Map :
- (i)  $AB + BC$
- (ii)  $(A + \overline{B})(\overline{B} + C)$ . 2½
- (C) What is shift register ? Explain 3-bit left shift register. 2½
- (D) Explain static RAM. 2½