

Bachelor of Science (B.Sc.I.T.) Semester—II (C.B.S.) Examination

FUNDAMENTALS OF DIGITAL ELECTRONICS

Paper—I

Time : Three Hours]

[Maximum Marks : 50

N.B. :— (1) All questions are compulsory and carry equal marks.

(2) Draw neat diagrams wherever necessary.

EITHER

1. (A) Explain the method of converting decimal number into its binary equivalent. 5
- (B) Obtain the following conversions :
 - (i) $(24)_{10} = (\quad)_2$
 - (ii) $(10110)_2 = (\quad)_{10}$
 - (iii) $(101)_{10} = (\quad)_2$
 - (iv) $(FA0)_{16} = (\quad)_8$. 5

OR

- (C) Explain XS-3 code. What are its uses ? 5
- (D) How does other codes differ from XS-3 code ? Explain. 5

EITHER

2. (A) Explain EX-OR gate using basic gates. 5
- (B) Design AND, OR, NOT and NOR gates only using NAND gates. 5

OR

- (C) State and prove De Morgan's theorem. 5
- (D) What is the use of K-map ? Explain. 5

EITHER

3. (A) Draw half adder circuit and explain. 5
- (B) What is a multiplexer ? Explain with an example. 5

OR

- (C) Explain the construction of a 4-bit asynchronous counter with timing diagram. 5
- (D) Draw RSFF using NOR gates and explain its working. 5

EITHER

4. (A) Explain volatile and non-volatile memory. 5
(B) Write a note on Cache Memory. 5

OR

- (C) Explain the difference between Hard disk and Optical disk. 5
(D) Explain difference between semiconductor and magnetic memory. 5
5. (A) Explain the method of subtraction of two binary numbers using 2's complement method. 2½
(B) Construct X-OR gate using NOR gates. 2½
(C) What is race around condition ? How to avoid it ? Explain. 2½
(D) Draw a block diagram of computer and explain in brief. 2½