

**Bachelor of Science (B.Sc.I.T.) Semester—II Examination****FUNDAMENTALS OF DIGITAL ELECTRONICS****Paper—I**

Time : Three Hours]

[Maximum Marks : 50

**N.B. :—** (1) All questions are compulsory and carry equal marks.

(2) Draw a well labelled diagram wherever necessary.

**EITHER**

1. (a) What is a number system ? Explain how positive and negative numbers are represented in binary number system with examples. 5
- (b) Do as directed :
  - (i)  $(1FA3.30)_{16} = ( ? )_2$
  - (ii)  $(10101011.1011)_2 = ( ? )_8$ . 5

**OR**

- (c) What is grey code ? Explain the method of converting binary number into grey code with suitable examples. 5
- (d) What is parity code ? What are its types ? Explain how it is useful in error finding ? 5

**EITHER**

2. (a) Explain the construction and working of Ex-OR gate using basic gates. How does it differ from OR gate ? 5
- (b) Construct the following gates using NAND gate exclusively :
  - (i) NOT gate
  - (ii) NOR gate
  - (iii) AND gate. 5

**OR**

- (c) State and prove De-Morgan's theorem for three variables using Truth table. 5
- (d) What is K-map ? Simplify the following expression using K-map :
 
$$f(A, B, C) = \sum m(0, 1, 4, 6, 7) + \sum d(2, 5)$$
 5

**EITHER**

3. (a) What is adder circuit ? Explain the construction and working of half adder circuit using gates. 5
- (b) What is decoder ? Explain the construction and working of 2 : 4 decoder using gates. Give any one application of decoder circuit. 5

**OR**

- (c) What is Flip-Flop ? Explain construction and working of D-FF using logic gates. 5
- (d) What is asynchronous counter ? Explain the construction and working of 3 bit ripple counter with truth table. 5

**EITHER**

4. (a) What is memory ? Differentiate between RAM and ROM. 5
- (b) What is hard disk ? Explain its construction and working with suitable diagram. 5

**OR**

- (c) Write a short note on Cache memory. 5
- (d) What is I/O device ? Explain any one I/O device in brief. 5
5. Attempt **all** :
- (a) Write a short note on ASCII Code. 2½
- (b) Explain the following terms related to K-map :
- (i) SOP
- (ii) POS 2½
- (c) What is preset and clear terminals in Flip-Flop ? What are their use in circuit ? 2½
- (d) Explain the concept of capacity of memory with suitable example. 2½