

Bachelor of Science (B.Sc. I.T.) Semester—II (C.B.S.) Examination
FUNDAMENTALS OF DIGITAL ELECTRONICS
Paper—I

Time : Three Hours]

[Maximum Marks : 50

Note :— (1) **ALL** questions are compulsory.

(2) Draw neat labelled diagrams wherever necessary.

EITHER

1. (a) Explain double dabble method of converting decimal number into its binary equivalent. 5
- (b) What are binary codes ? Explain gray code with suitable example. 5

OR

- (c) Do as directed :
 - (i) $(1101)_{10} = ()_2$
 - (ii) $(234)_7 = ()_{10}$. 5
- (d) Explain 2's complement method of number representation. 5

EITHER

2. (a) Construct AND, OR and NOR gates using only NANO gates. 5
- (b) State and prove De-Morgan's theorem. 5

OR

- (c) What is a k-map ? How does it help in reducing the equations in SOP form ? 5
- (d) Explain Quine McClusky method. 5

EITHER

3. (a) What is a multiplexer ? Explain the working of 4 : 1 multiplexer with circuit diagram. 5
- (b) Explain the working of a 3-bit asynchronous counter. 5

OR

- (c) What is full adder ? Explain the working of a full adder circuit with neat diagram. 5
- (d) Explain the working of JKMSFF with circuit diagram. 5

EITHER

4. (a) Explain ROM and EPROM. 5
- (b) Explain the organization of a hard disk. 5

OR

- (c) Write a note on any two I/O devices. 5
- (d) What is cache memory ? Explain. 5

5. Attempt **all** :

- (a) What is an ASCII code ? Explain. 2½
- (b) Why NOR gates is called as universal building blocks ? Explain. 2½
- (c) What is a demultiplexer ? Explain. 2½
- (d) What is RAM ? Explain. 2½